

Solutions to Homework 7

1. At $t = 0$, a current of 2 amperes flows in an RLC circuit with resistance $R = 4$ ohms, inductance $L = 0.05$ henrys, and capacitance $C = 0.008$ farads. The initial charge on the capacitor is -1 coulomb, and there is no impressed voltage for $t > 0$.

- (a) Find the current flowing in the circuit at $t > 0$.

Solution. From the information given by the problem statement, we have

$$\begin{aligned}Q(0) &= -1 \text{ coulomb,} \\Q'(0) &= I(0) = 2 \text{ amperes,} \\R &= 4 \text{ ohms,} \\L &= 0.05 \text{ henrys,} \\C &= 0.008 \text{ farads,} \\E(t) &= 0.\end{aligned}$$

So the differential equation for the RLC circuit

$$LQ'' + RQ' + \frac{1}{C}Q = E(t)$$

becomes

$$0.05Q'' + 4Q' + \frac{1}{0.008}Q = 0.$$

By substituting $Q = e^{rt}$ and its first and second derivatives $Q' = re^{rt}$, $Q'' = r^2e^{rt}$ and recognizing $e^{rt} \neq 0$, we obtain the auxiliary equation

$$0.05r^2 + 4r + \frac{1}{0.008} = 0,$$

which has complex roots $r = -40 \pm 30i$. So our general solution is

$$\begin{aligned}Q(t) &= c_1e^{(-40-30i)t} + c_2e^{(-40+30i)t} \\&= e^{-40t}(c_1e^{-30it} + c_2e^{30it}) \\&= e^{-40t}(c_1 \cos(30t) + c_2 \sin(30t)) \\&= c_1e^{-40t} \cos(30t) + c_2e^{-40t} \sin(30t),\end{aligned}$$

where c_1, c_2 are arbitrary constants. Also, the first derivative of $Q(t)$ is

$$\begin{aligned}Q'(t) &= c_1(e^{-40t} \cos(30t))' + c_2(e^{-40t} \sin(30t))' \\&= c_1(-40e^{-40t} \cos(30t) - 30e^{-40t} \sin(30t)) \\&\quad + c_2(-40e^{-40t} \sin(30t) + 30e^{-40t} \cos(30t)) \\&= (-40c_1 + 30c_2)e^{-40t} \cos(30t) \\&\quad + (-30c_1 - 40c_2)e^{-40t} \sin(30t).\end{aligned}$$

Now, $Q(0) = -1$ implies $c_1 = -1$, and $Q'(0) = 2$ with $c_1 = -1$ imply $c_2 = -\frac{19}{15}$. Therefore, the charge for all $t > 0$ is

$$\begin{aligned} Q(t) &= c_1 e^{-40t} \cos(30t) + c_2 e^{-40t} \sin(30t) \\ &= -e^{-40t} \cos(30t) - \frac{19}{15} e^{-40t} \sin(30t), \end{aligned}$$

and the current flowing in the circuit for all $t > 0$ is

$$\begin{aligned} I(t) &= Q'(t) \\ &= (-40c_1 + 30c_2)e^{-40t} \cos(30t) \\ &\quad + (-30c_1 - 40c_2)e^{-40t} \sin(30t) \\ &= \left(-40(-1) + 30\left(-\frac{19}{15}\right)\right) e^{-40t} \cos(30t) \\ &\quad + \left(-30(-1) - 40\left(-\frac{19}{15}\right)\right) e^{-40t} \sin(30t) \\ &= \boxed{2e^{-40t} \cos(30t) + \frac{242}{3} e^{-40t} \sin(30t)}. \end{aligned}$$

□

(b) Show that the current is a transient solution.

Solution. To show that the current is a transient solution for the case $E(t) = 0$, we need to show

$$\begin{aligned} \lim_{t \rightarrow \infty} Q(t) &= 0, \\ \lim_{t \rightarrow \infty} I(t) &= 0. \end{aligned}$$

First, we have

$$\begin{aligned} Q(t) &= -e^{-40t} \cos(30t) - \frac{19}{15} e^{-40t} \sin(30t) \\ &\leq e^{-40t} + \frac{19}{15} e^{-40t} \\ &= \frac{34}{15} e^{-40t} \end{aligned}$$

and

$$\begin{aligned} Q(t) &= -e^{-40t} \cos(30t) - \frac{19}{15} e^{-40t} \sin(30t) \\ &\geq -e^{-40t} - \frac{19}{15} e^{-40t} \\ &= -\frac{34}{15} e^{-40t}. \end{aligned}$$

In other words, we have

$$-\frac{34}{15} e^{-40t} \leq Q(t) \leq \frac{34}{15} e^{-40t}.$$

By the Squeeze Theorem, we conclude $\lim_{t \rightarrow \infty} Q(t) = 0$. Next, we have

$$\begin{aligned} I(t) &= 2e^{-40t} \cos(30t) + \frac{242}{3} e^{-40t} \sin(30t) \\ &\leq 2e^{-40t} + \frac{242}{3} e^{-40t} \\ &= \frac{248}{3} e^{-40t} \end{aligned}$$

and

$$\begin{aligned} I(t) &= 2e^{-40t} \cos(30t) + \frac{242}{3} e^{-40t} \sin(30t) \\ &\geq -2e^{-40t} - \frac{242}{3} e^{-40t} \\ &= -\frac{248}{3} e^{-40t}. \end{aligned}$$

In other words, we have

$$-\frac{248}{3} e^{-40t} \leq I(t) \leq \frac{248}{3} e^{-40t}.$$

By the Squeeze Theorem, we conclude $\lim_{t \rightarrow \infty} I(t) = 0$. □

2. Consider an RLC circuit with resistance $R = 2$ ohms, inductance $L = 0.1$ henrys, and capacitance $C = 0.01$ farads. The initial charge and current is 1 coulomb and 10 amperes, respectively. Assume that there is an impressed voltage of $3 \cos(50t) - 6 \sin(50t)$.

(a) Find the particular solution of the current, in other words, steady-state solution of the current.

Solution. From the information given by the problem statement, we have

$$\begin{aligned} Q(0) &= 1 \text{ coulomb,} \\ Q'(0) &= I(0) = 10 \text{ amperes,} \\ R &= 2 \text{ ohms,} \\ L &= 0.1 \text{ henrys,} \\ C &= 0.01 \text{ farads,} \\ E(t) &= 3 \cos(50t) - 6 \sin(50t). \end{aligned}$$

So the differential equation for the RLC circuit

$$LQ'' + RQ' + \frac{1}{C}Q = E(t)$$

becomes

$$0.1Q'' + 2Q' + \frac{1}{0.01}Q = 0.$$

Let Q_p be the particular solution of the form

$$Q_p(t) = A \cos(50t) + B \sin(50t),$$

whose first and second derivatives are

$$\begin{aligned}Q'_p(t) &= -50A \sin(50t) + 50B \cos(50t), \\Q''_p(t) &= -2500A \cos(50t) - 2500B \sin(50t).\end{aligned}$$

By substituting these expressions into our differential equation for the RLC circuit, we obtain

$$\begin{aligned}0.1[-2500A \cos(50t) - 2500B \sin(50t)] \\+ 2[-50A \sin(50t) + 50B \cos(50t)] \\+ \frac{1}{0.01}[A \cos(50t) + B \sin(50t)] &= 3 \cos(50t) - 6 \sin(50t),\end{aligned}$$

which is equivalent to

$$\begin{aligned}-250A \cos(50t) - 250B \sin(50t) \\- 100A \sin(50t) + 100B \cos(50t) \\+ 100A \cos(50t) + 100B \sin(50t) &= 3 \cos(50t) - 6 \sin(50t),\end{aligned}$$

which is equivalent to

$$(-150A + 100B) \cos(50t) + (-100A - 150B) \sin(50t) = 3 \cos(50t) - 6 \sin(50t),$$

from which we equate the terms to obtain

$$\begin{aligned}-150A + 100B &= 3, \\-100A - 150B &= -6,\end{aligned}$$

from which we can simultaneously solve to find $A = \frac{3}{650}$, $B = \frac{12}{325}$. Therefore, the particular solution of the current for all $t > 0$ is

$$\begin{aligned}I_p(t) &= Q'_p(t) \\&= -50A \sin(50t) + 50B \cos(50t) \\&= -50 \left(\frac{3}{650} \right) \sin(50t) + 50 \left(\frac{12}{325} \right) \cos(50t) \\&= -\frac{3}{13} \sin(50t) + \frac{24}{13} \cos(50t) \\&= \boxed{\frac{24}{13} \cos(50t) - \frac{3}{13} \sin(50t)}.\end{aligned}$$

□

(b) Does the initial charge and current affect the steady-state current?

Solution. No, because the steady-state current—a.k.a. the particular solution of the current—does not depend on the values of $Q(0)$ and $I(0) = Q'(0)$. □

3. Consider the same RLC circuit as in problem 2, with impressed voltage of $6 \cos(10t) - 3 \sin(10t)$.

- (a) Find the particular solution of the current, in other words, steady-state solution of the current.

Solution. From the information given by the statements of Problems 2 and 3, we have

$$\begin{aligned} Q(0) &= 1 \text{ coulomb,} \\ Q'(0) &= I(0) = 10 \text{ amperes,} \\ R &= 2 \text{ ohms,} \\ L &= 0.1 \text{ henrys,} \\ C &= 0.01 \text{ farads,} \\ E(t) &= 6 \cos(10t) - 3 \sin(10t). \end{aligned}$$

So the differential equation for the RLC circuit

$$LQ'' + RQ' + \frac{1}{C}Q = E(t)$$

becomes

$$0.1Q'' + 2Q' + \frac{1}{0.01}Q = 0.$$

Let Q_p be the particular solution of the form

$$Q_p(t) = A \cos(10t) + B \sin(10t),$$

whose first and second derivatives are

$$\begin{aligned} Q'_p(t) &= -10A \sin(10t) + 10B \cos(10t), \\ Q''_p(t) &= -100A \cos(10t) - 100B \sin(10t). \end{aligned}$$

By substituting these expressions into our differential equation for the RLC circuit, we obtain

$$\begin{aligned} &0.1[-100A \cos(10t) - 100B \sin(10t)] \\ &+ 2[-10A \sin(10t) + 10B \cos(10t)] \\ &+ \frac{1}{0.01}[A \cos(10t) + B \sin(10t)] = 6 \cos(10t) - 3 \sin(10t), \end{aligned}$$

which is equivalent to

$$\begin{aligned} &-10A \cos(50t) - 10B \sin(50t) \\ &-20A \sin(50t) + 20B \cos(50t) \\ &+ 100A \cos(50t) + 100B \sin(50t) = 6 \cos(10t) - 3 \sin(10t), \end{aligned}$$

which is equivalent to

$$(90A + 20B) \cos(10t) + (-20A + 90B) \sin(10t) = 6 \cos(10t) - 3 \sin(10t),$$

from which we equate the terms to obtain

$$\begin{aligned} 90A + 20B &= 6, \\ -20A + 90B &= -3, \end{aligned}$$

from which we can simultaneously solve to find $A = \frac{6}{85}$, $B = -\frac{3}{170}$. Therefore, the particular solution of the current for all $t > 0$ is

$$\begin{aligned}
 I_p(t) &= Q'_p(t) \\
 &= -10A \sin(10t) + 10B \cos(10t) \\
 &= -10 \left(\frac{6}{85} \right) \sin(10t) + 10 \left(-\frac{3}{170} \right) \cos(10t) \\
 &= -\frac{12}{17} \sin(10t) - \frac{3}{17} \cos(10t) \\
 &= \boxed{-\frac{3}{17} \cos(10t) - \frac{12}{17} \sin(10t)}.
 \end{aligned}$$

□

- (b) Compare the amplitude of the steady-state current between problem 2 and 3. Which is larger?

Solution. In general, we can express the steady-state current as a single sine wave:

$$\begin{aligned}
 I_p(t) &= \alpha \sin(kt + \beta) \\
 &= \alpha [\sin(kt) \cos \beta + \cos(kt) \sin \beta] \\
 &= \alpha \sin(kt) \cos \beta + \alpha \cos(kt) \sin \beta \\
 &= [\alpha \sin \beta] \cos(kt) + [\alpha \cos \beta] \sin(kt),
 \end{aligned}$$

where α denotes the amplitude of the steady-state current.

For Problem 2: We have

$$[\alpha \sin \beta] \cos(50t) + [\alpha \cos \beta] \sin(50t) = I_p(t) = \frac{24}{13} \cos(50t) - \frac{3}{13} \sin(50t),$$

from which we equate the terms to obtain

$$\begin{aligned}
 \alpha \sin \beta &= \frac{24}{13}, \\
 \alpha \cos \beta &= -\frac{3}{13}.
 \end{aligned}$$

So we have

$$\begin{aligned}
 \alpha^2 &= \alpha^2 (\sin^2 \beta + \cos^2 \beta) \\
 &= (\alpha \sin \beta)^2 + (\alpha \cos \beta)^2 \\
 &= \left(\frac{24}{13} \right)^2 + \left(-\frac{3}{13} \right)^2 \\
 &= \frac{45}{13},
 \end{aligned}$$

from which we conclude that our amplitude is $\alpha = \sqrt{\frac{45}{13}} \approx 1.86$.

For Problem 3: We have

$$[\alpha \sin \beta] \cos(10t) + [\alpha \cos \beta] \sin(10t) = I_p(t) = \frac{3}{17} \cos(10t) - \frac{12}{17} \sin(10t),$$

from which we equate the terms to obtain

$$\begin{aligned}\alpha \sin \beta &= \frac{3}{17}, \\ \alpha \cos \beta &= -\frac{12}{17}.\end{aligned}$$

So we have

$$\begin{aligned}\alpha^2 &= \alpha^2(\sin^2 \beta + \cos^2 \beta) \\ &= (\alpha \sin \beta)^2 + (\alpha \cos \beta)^2 \\ &= \left(\frac{3}{17}\right)^2 + \left(-\frac{12}{17}\right)^2 \\ &= \frac{9}{17},\end{aligned}$$

from which we conclude that our amplitude is $\alpha = \sqrt{\frac{9}{17}} \approx 0.73$.

Therefore, we conclude that the amplitude of the steady-state current from Problem 2 is larger than that from Problem 3. \square

4. Find the Laplace transformation of the following functions and the range of s that it is valid.

(a) t^2

Solution. We already know from your professor's notes for the lecture on May 18, 2022 that the Laplace transform of t is $\mathcal{L}(t) = \frac{1}{s^2}$ for all $s > 0$. Using this, we find that the Laplace transform of t^2 is

$$\begin{aligned}\mathcal{L}(t^2) &= \int_0^{\infty} e^{-st} t^2 dt \\ &= -\frac{1}{s} t^2 e^{-st} \Big|_0^{\infty} + \frac{2}{s} \int_0^{\infty} t e^{-st} dt \\ &= -\frac{1}{s} (0 - 0^2 e^{-s(0)}) + \frac{2}{s} \mathcal{L}(t) \\ &= \frac{2}{s} \mathcal{L}(t) \\ &= \frac{2}{s} \frac{1}{s^2} \\ &= \boxed{\frac{2}{s^3}}\end{aligned}$$

for all $s > 0$. \square

(b) $e^{-2t} + 3e^t$

Solution. We already know from your professor's notes for the lecture on May 18, 2022 that the Laplace transform of t is $\mathcal{L}(e^{at}) = \frac{1}{s-a}$ for all $s > a$. In particular, we have

$$\begin{aligned}\mathcal{L}(e^{-2t}) &= \frac{1}{s+2}, & s > -2, \\ \mathcal{L}(e^t) &= \frac{1}{s-1}, & s > 1.\end{aligned}$$

Using these facts and the linearity of the Laplace transform, we find that the Laplace transform of $e^{-2t} + 3e^t$ is

$$\begin{aligned}\mathcal{L}(e^{-2t} + 3e^t) &= \mathcal{L}(e^{-2t}) + 3\mathcal{L}(e^t) \\ &= \frac{1}{s+2} + 3\frac{1}{s-1} \\ &= \boxed{\frac{4s+5}{(s-1)(s+2)}}\end{aligned}$$

for all $s > 1$. □

5. Find the Laplace transformation of the following functions and the range of s that it is valid.

(a) $\sin\left(t + \frac{\pi}{4}\right)$

Solution. We can rewrite

$$\begin{aligned}\sin\left(t + \frac{\pi}{4}\right) &= \sin t \cos\left(\frac{\pi}{4}\right) + \cos t \sin\left(\frac{\pi}{4}\right) \\ &= \sin t \frac{1}{\sqrt{2}} + \cos t \frac{1}{\sqrt{2}} \\ &= \frac{1}{\sqrt{2}}(\sin t + \cos t).\end{aligned}$$

Also, we already know from your professor's notes for the lecture on May 18, 2022 that the Laplace transforms of $\sin(\omega t)$ and $\cos(\omega t)$ are

$$\begin{aligned}\mathcal{L}(\sin(\omega t)) &= \frac{\omega}{s^2 + \omega^2}, & s > 0, \\ \mathcal{L}(\cos(\omega t)) &= \frac{s}{s^2 + \omega^2}, & s > 0.\end{aligned}$$

In particular, we have

$$\begin{aligned}\mathcal{L}(\sin t) &= \frac{1}{s^2 + 1}, & s > 0, \\ \mathcal{L}(\cos t) &= \frac{s}{s^2 + 1}, & s > 0.\end{aligned}$$

By the linearity of the Laplace transform, we find that the Laplace transform of $\sin\left(t + \frac{\pi}{4}\right)$ is

$$\begin{aligned}\mathcal{L}\left(\sin\left(t + \frac{\pi}{4}\right)\right) &= \mathcal{L}\left(\frac{1}{\sqrt{2}}(\sin t + \cos t)\right) \\ &= \frac{1}{\sqrt{2}}(\mathcal{L}(\sin t) + \mathcal{L}(\cos t)) \\ &= \frac{1}{\sqrt{2}}\left(\frac{1}{s^2 + 1} + \frac{s}{s^2 + 1}\right) \\ &= \frac{1}{\sqrt{2}}\frac{1 + s}{s^2 + 1} \\ &= \boxed{\frac{s + 1}{\sqrt{2}(s^2 + 1)}}\end{aligned}$$

for all $s > 0$. □

(b) $\sin^2(t)$

Solution. We already know from your professor's notes for the lecture on May 18, 2022 that the Laplace transforms of 1 and $\cos(\omega t)$ are

$$\begin{aligned}\mathcal{L}(1) &= \frac{1}{s}, \quad s > 0, \\ \mathcal{L}(\cos(\omega t)) &= \frac{s}{s^2 + \omega^2}, \quad s > 0.\end{aligned}$$

In particular, we have

$$\begin{aligned}\mathcal{L}(1) &= \frac{1}{s}, \quad s > 0, \\ \mathcal{L}(\cos(2t)) &= \frac{s}{s^2 + 4}, \quad s > 0.\end{aligned}$$

By the linearity of the Laplace transform, we find that the Laplace transform of $\sin^2 t$ is

$$\begin{aligned}\mathcal{L}(\sin^2 t) &= \mathcal{L}\left(\frac{1}{2}(1 - \cos(2t))\right) \\ &= \frac{1}{2}(\mathcal{L}(1) - \mathcal{L}(\cos(2t))) \\ &= \frac{1}{2}\left(\frac{1}{s} - \frac{s}{s^2 + 4}\right) \\ &= \frac{1}{2}\frac{4}{s(s^2 + 4)} \\ &= \boxed{\frac{2}{s(s^2 + 4)}}\end{aligned}$$

for all $s > 0$. □